



AR - 0636

B.C.A. Part - I Semester - II

Digital Techniques - II Paper - 2ST3

P. Pages : 4

Time : Three Hours

Max. Marks : 60

- Notes :
1. All questions are compulsory.
 2. Draw neat diagrams wherever necessary.

Either

1. A) Draw logic diagram of a CK-RSFF and explain its working. Draw its truth table. **6**
- B) What is Multivibrator? Explain working of transistorised astable Multivibrator. **6**

OR

2. A) Explain the working of JKFF with logic diagrams and truth table. **6**
- B) What is race around condition in JKFF? Explain in detail. **4**
- C) State uses of PRESET and CLEAR terminals in flip flops. **2**

Either

9. A) What is A/D and D/A converter? Explain the need of data converters. **4**
- B) Explain the working of R-2 R type D/A converter. **4**
- C) Draw block diagram of counter type A/D converter and explain its working. **4**

OR

10. A) Explain the working of weighted resistor type D/A converter. **4**
- B) Draw block diagram of successive approximation type A/D converter and explain its working. **4**
- C) Draw and explain IC ADC 0808 with pin diagram. **4**

Either

3. A) Define i) Counter 4
 ii) Asynchronous counter
 iii) Synchronous counter
 iv) Decade counter

B) Explain working of 3- bit asynchronous counter. 4

C) Draw pin diagram of IC 7490 and explain functions of all pins. 4

OR

4. A) Define i) Modulus of a counter. 4
 ii) Up counter
 iii) Down counter
 iv) Modified counter.

B) Draw circuit diagram of a 3-bit synchronous counter and explain its working. 4

C) State applications of counters. 4

Either

5. A) What is shift register? Explain the working of 4-bit SISO shift register. 6

B) Explain the working of Ring counter with neat diagram. 6

OR

6. A) Draw block diagram of PISO shift register and explain its working. 6

B) Draw block diagram of IC 7495 and explain it in detail. 6

Either

7. A) What is memory? Give classification of memories. 4

B) Explain construction of floppy disk. 4

C) Differentiate between RAM and ROM. 4

OR

8. A) What is CD-ROM? Explain the working of CD-ROM. 4

B) With the help of neat diagram explain the construction of Winchester disk. 4

C) Explain PROM and EPROM in detail. 4