

B.E. Fourth Semester (Electronics & Telecommunication) (New)

Digital Electronics : 4 ET 04

P. Pages : 2

Time :



AU - 2590

Max. Marks : 80

- Notes :
1. All question carry equal marks.
 2. Answer **three** question from section A and **three** question from section B.
 3. Assume suitable data wherever necessary.
 4. Illustrate your answer necessary with the help of neat sketches.
 5. Use of pen Blue/Black ink/refill only for writing book.

1. a) Explain in brief Transistor-Transistor logic (TTL) circuit with active pull up arrangements. Verify the logic operations given by TTL. 7

- b) Perform the following. 7

- i) Convert $(1011011)_2$ to Gray code
- ii) Convert $(28F)_{16}$ to octal
- iii) $(75)_{10} - (57)_{10}$ by 2's complement method.

OR

2. a) Minimize the following logical expressions by Boolean Algebra 8

- i) $B \oplus (B \oplus AC) = AC$
- ii) $ABC + B\bar{C}D + \bar{A}BC = BC + BD$

- b) Explain the following characteristics of digital IC's. 6

- i) Noise Margin
- ii) Figure of merit
- iii) Fanin and Fanout

3. a) Minimize the following logic function and realize using NAND gates only. 7

$$f_1(A, B, C, D) = \sum m(1, 3, 5, 8, 9, 11, 15) + d(2, 13)$$

- b) Design the combinational circuit for full adder and implement it using suitable gates. 6

OR

4. a) Design and explain one digit BCD adder circuit using 4-bit adder IC 74LS83 and required gates. Explain with the help of suitable example. 7

- b) Design binary to gray cod converter circuit using suitable gates. 6

5. a) Implement the following logical expression using 8:1 MUX 7

$$F = \sum m(0, 1, 2, 3, 4, 10, 11, 14, 15)$$

- b) Design 5-line to 32 line decoder circuit using 4-line to 16-line decoders and suitable gate. 6

OR


6. a) Design 5-bit comparator using single 7485 IC and suitable gate. Also explain its operation. 7

- b) Compare ROM, PLA and PAL 6

7. a) What is Race around condition? How it is overcome? Explain master-slave J-K flip flop with proper table. 7
- b) Design 4-bit parallel in serial out right shift register using D-Flip Flops and suitable gates. 6

OR

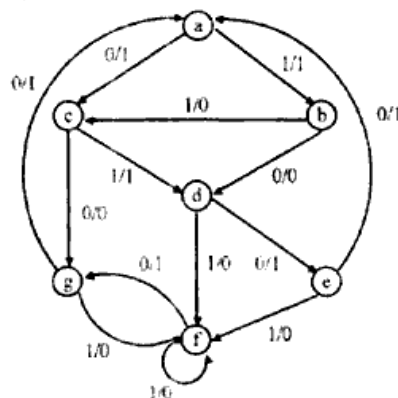
8. a) State differences between synchronous and asynchronous counters. 5
- b) Design 2-bits asynchronous up counter using negative edge triggered T-Flip Flops and explain its operation with proper wave forms. 8
9. a) Obtain reduced state table and reduced state diagram for the sequential machine whose state diagram is shown below. 6



- b) Draw the state diagram and state table for a Moore type sequence detector to detect the sequence 110. 8

OR

 10. Design a clocked sequential circuit using T-Flip Flops and suitable gates for the state diagram given below. 13



11. a) Explain in brief- 8
- i) PROM ii) EPROM
- iii) EEPROM iv) NVRAM
- b) Explain the working of dynamic RAM cell. 5

OR

12. a) Explain the read cycle timing parameters of a memory using proper timing diagram. 6
- b) With neat circuit diagram explain the operation of bipolar static RAM cell. 7
