

AU – 2722

Fifth Semester B. E. (Information Technology) (CGS) Examination

DIGITAL INTEGRATED CIRCUITS

Paper – 5 IT 02

(USC – 10731)

P. Pages : 3

Time : Three Hours]

[Max. Marks : 80

- Note :** (1) Assume suitable data wherever necessary.
(2) Illustrate your answer wherever necessary with the help of neat sketches.
(3) Use pen of Blue/Black ink/refill only for writing the answer book.

1. (A) Convert the equation in sum of Minterm form and implement using only NAND gates :

$$F = (xy + z) (xz + y) \quad 6$$

- (B) Draw the circuit and explain the operation of TTL NAND gate. 7

OR

2. (A) Convert the equation in canonical POS form and implement using only NOR gates.

$$F = xy + \bar{x}z \quad 7$$

- (B) Explain following characteristics of digital ICs.

(i) Propagation Delay.

(ii) Noise Margin. 6

3. (A) Minimize using k-map :

$$f = \Sigma m(6, 9, 13, 18, 19, 25, 27, 29, 31) + d(2, 3, 11, 15, 17, 24, 28) \quad 7$$

- (B) Simplify using k-map and realize the minimized equation using NOR gates.

$$F = \pi M(0, 7, 9, 13, 27, 31) \cdot d(2, 4, 8, 18, 30) \quad 7$$

AU-2722

P.T.O.

OR

4. (A) Simplify using k-map and realize using NAND gates.
 $f = \Sigma m(0, 1, 5, 6, 8, 9, 11, 13) + d(7, 10, 12)$ 6
- (B) Find the PIS and EPIs, using tabulation method.
 $f = \Sigma m(1, 3, 7, 11, 15) + d(0, 2, 5)$ 8
5. (A) Implement a full Adder using two Half adder and a logic gate. 6
- (B) Realize a function with multilevel NAND circuit.
 $f = (\bar{A} + B) (C + DE)$ 7

OR

6. (A) Design and draw a 4-bit binary to Excess-3 code converter. 7
- (B) Design and draw a 4-bit odd parity checker. 6
7. (A) Draw and explain a BCD Adder using 4 bit binary adder. 7
- (B) Implement a function $f = \Sigma m(0, 2, 5, 6, 9, 11, 14)$ using a 8:1 MUX. 7

OR

8. (A) A combinational ckt is defined by,
 $F_1 = \Sigma m(2, 5, 6), F_2 = \Sigma m(1, 4, 5, 7)$ Implement it using a 3:8 decoder and logic gates. 7
- (B) Implement the following function with PLA.
 $F_1 = \bar{A}\bar{B} + BC$ and
 $F_2 = A\bar{C} + BC$ 7
9. (A) Explain how J-K D and T flip flops can be obtained from S-R flip flop. Also give their excitation tables. 6

- (B) Design a 4 bit synchronous counter using T-flip flop. 7

OR

10. (A) With the help of truth table draw the state diagram for J-K flip flop. 6

- (B) Design and draw a Mod 5 Asynchronous counter. 7

11. (A) Draw a 5 bit shift register that enables the Read and write operations in both serial as well as parallel mode. Explain its function in brief. 7

- (B) Draw the structure of static RAM(SRAM) cell and explain its function. 6

OR

12. (A) What are types of RAMs ? Explain in brief. 6

- (B) What is ASM ? Explain various blocks of ASM chart. 7



<http://www.sgbauonline.com>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से