

AQ - 2648

First Semester M. Sc. (Applied Electronics) (CBS) Examination

(New)

**ELECTRICAL ENGINEERING AND NETWORK ANALYSIS**

I AE I

P. Pages : 6


Time : Three Hours ]

[ Max. Marks : 80

- Note :** (1) Separate answer book must be used for each section in the subject Geology, Engineering material of civil branch and Separate answer book must be used for Section A and B in Pharmacy and Cosmetic Tech.
- (2) All question carry equal marks.
- (3) Due credit will be given to neatness and adequate dimensions.
- (4) Assume suitable data wherever necessary.
- (5) Diagrams and Chemical equations should be given wherever necessary.
- (6) Retain the construction lines.
- (7) Illustrate your answer wherever necessary with the help of neat sketches.
- (8) Use of slide rule, logarithmic tables, Steam tables, Mollier's Chart, Drawing instrument, Thermodynamic table for moist air, Psychrometric Charts and Refrigeration charts is permitted.
- (9) Discuss the reaction, mechanism wherever necessary.
- (10) Use pen of Blue/Black ink/refill only for writing the answer book.

**SECTION A**

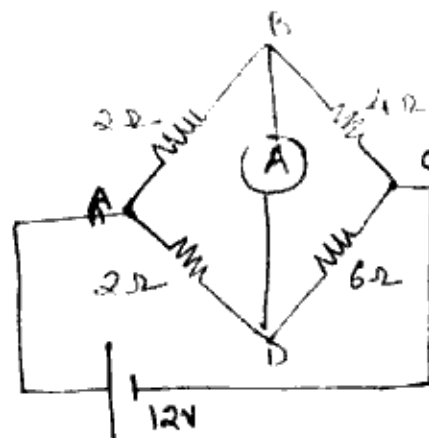1. (a) Derive the relationship for conversion from delta to star. 6
- (b) Determine the current through the ammeter of resistance 2 ohms connected in the Wheatstone bridge between terminals A and B.



8

OR

2. (a) Define the terms :—

(i) RMS value

(ii) Average value

(iii) Instantaneous value

(iv) Phase

8

(b) An induction circuit supplied with 100 V at 50 Hz is found to take 10 A and when supplied with 100 V at 200 Hz, it takes 5A. Determine the circuit constants assuming sinusoidal current.

6

3. (a) Derive the expression for induced emf in single phase transformer.

3

(b) Practical transformer differs from an ideal transformer. Explain.


4

(c) What are the different types of losses in a transformer ?

6


OR

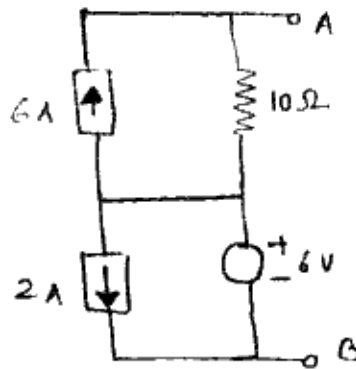4. (a) Reduce the network to a single source and single resistance.




6

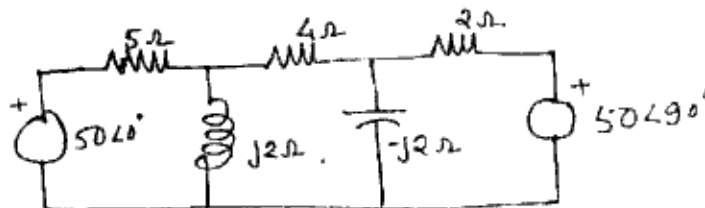(b) In the network shown below determine currents in the impedances  $j2\Omega$  and  $-j2\Omega$  using nodal analysis.




7

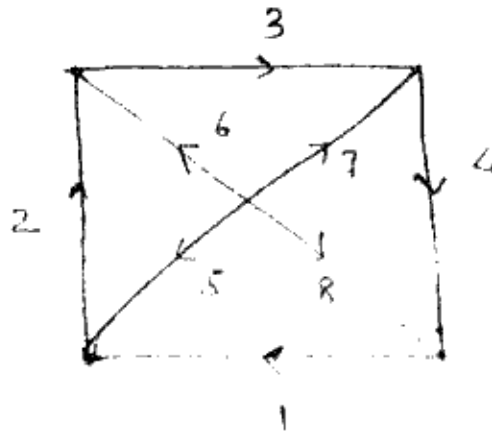5. (a) For the network given below develop the cut-set schedule and write the equations expressing branch voltages in terms of tree branch voltages.



7

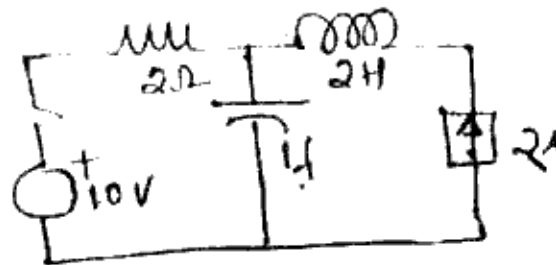
- (b) Explain Duality. Draw the dual of the network given below.



6

OR

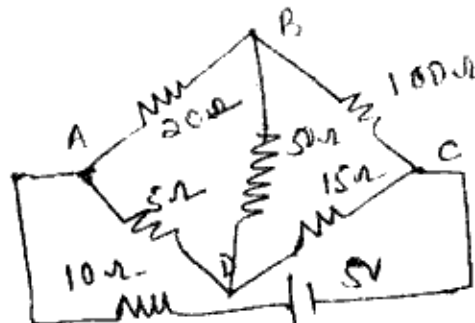
6. (a) Explain the terms (i) Tree (ii) Tie set matrix (iii) Reduced incidence matrix with examples. 6
- (b) Draw the graph and tree and hence current through  $50\Omega$  resistance by using current variable method.



7

## SECTION B

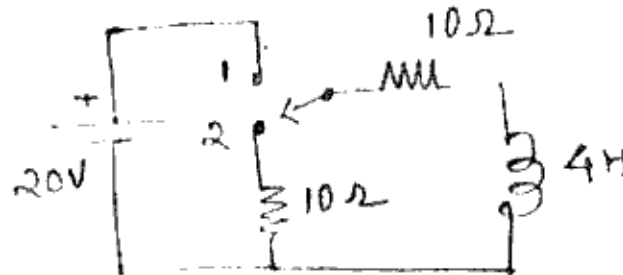7. (a) A circuit shown below is initially under steady condition. Switch is moved from position 1 to 2 at  $t = 0$ , find current through  $L$  after switching.



7


- (b) Find the initial and final value of current

$$I(S) = \frac{17s^3 + 7s^2 + s + 6}{s^5 + 3s^4 + 5s^3 + 4s^2 + 2s}$$

6

OR

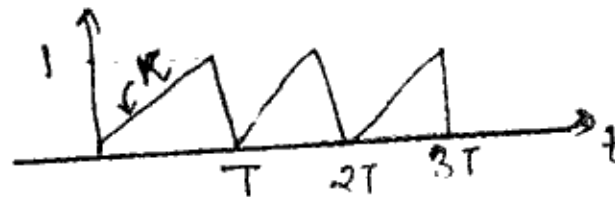8. (a) Find the Laplace transform of periodic wave shown in fig.




7

- (b) Obtain the response of the R-L-C series circuit subjected to input  $f(t) = Su(t-2)$


7

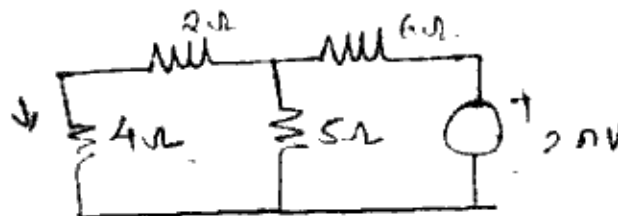9. (a) Verify reciprocity theorem for given network below.



7

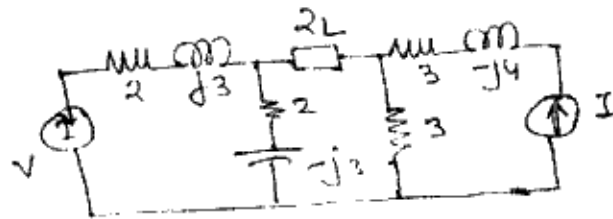
- (b) Find out the value of  $2L$  shown in fig. below for maximum power transfer.



7


OR

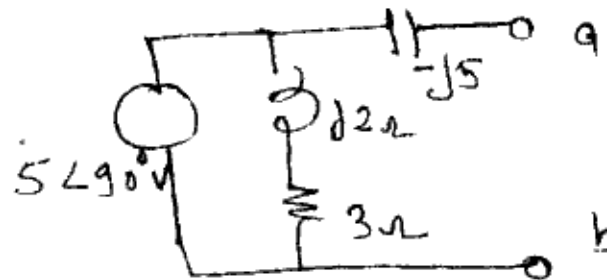10. (a) Obtain the Thevenin's equivalent for the given network points a and b in fig below.



7

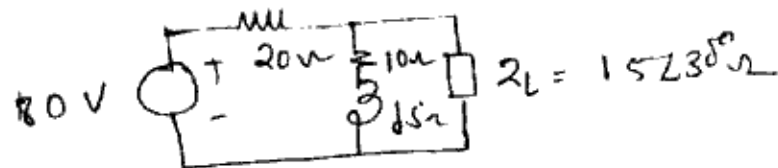- (b) Using Norton's theorem find the current through load impedance  $2L$  in fig. 7(a)




7

11. (a) Derive the condition of reciprocity for AB CD parameters.

6

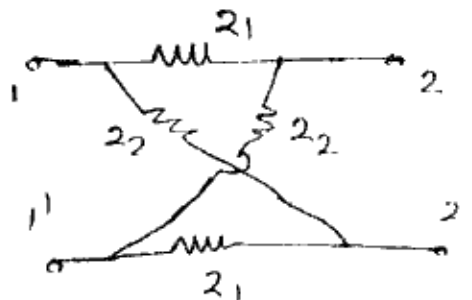
- (b) Find the 2-parameters for the following network given below.



7

OR

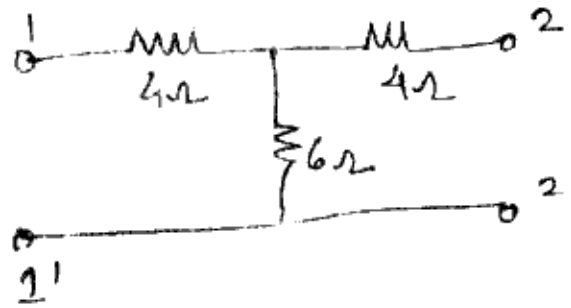12. (a) What is output impedance ? Determine the output impedance in terms of transmission parameters. 7
- (b) Find hybrid parameters for the network shown below.



Comment on the symmetry and reciprocity.

6

