

M.Sc. First Semester (Applied Electronics) (New) (CBS)
15001 : Electrical Engineering & Network Analysis : 1 AE 1

P. Pages : 4

Time : Three Hours




AV - 3291


Max. Marks : 80

- Notes : 1. Due credit will be given to neatness and adequate dimensions.
 2. Illustrate your answer necessary with the help of neat sketches.

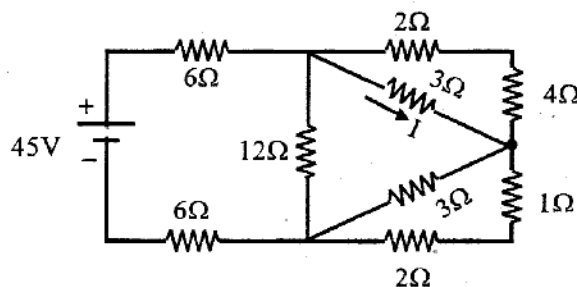1. a) Find current I in the network shown in figure. 7



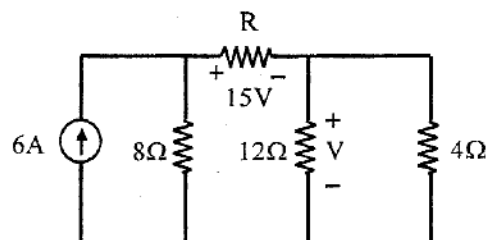- b) Find 'R' and V in the network shown in figure. 6




OR

2. a) In a given R – L circuit, $R = 2.5\Omega$, $L = 0.2H$ Find current through circuit and power factor if a-c voltage of $230 \angle 30^\circ$, 50Hz is applied. 6

- b) A certain inductive coil takes 15A when supply voltage is 230V, 50Hz, If frequency is changed to 40Hz, the current increases to 17.2A Calculate resistance and Inductance of a coil. 7


3. a) Derive the EMF equation of transformer. 7

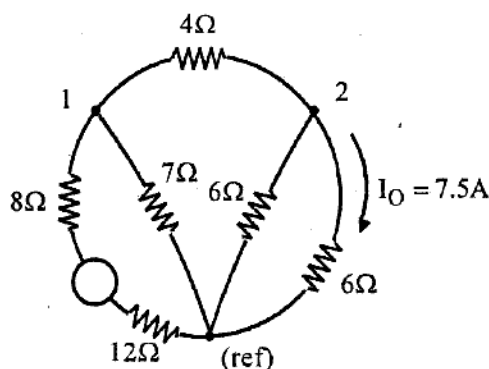- b) For the network shown in figure. Find V_s , which makes $V_o = 7.5A$. (nodal analysis) 7




OR

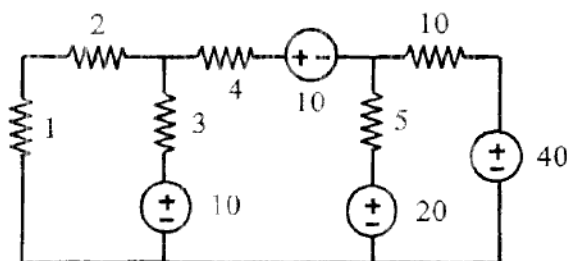4. a) For the circuit shown obtain current through each element by Mesh analysis. 7




- b) Explain in brief the losses in transformer and voltage regulation of transformer. 7

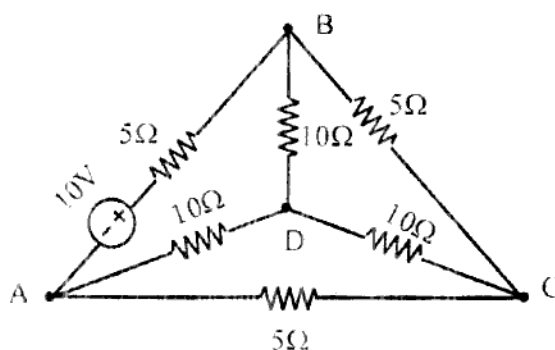5. Draw the oriented graph of ckt shown in fig. and write down network equilibrium equations in matrix form. Using KVL (Tree – set – Basis) 13





OR

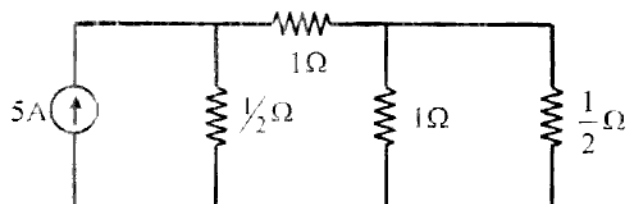6. For the network shown in fig. Write down the f-cut set matrix and Hence obtain equilibrium equations. 13



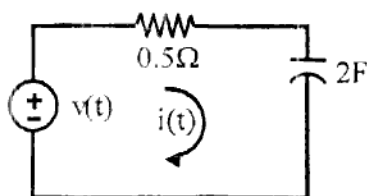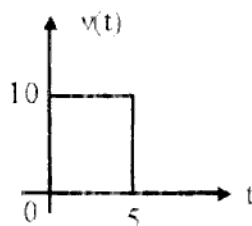7. a) Determine the current $i(t)$ through the circuit. 7




- b) Determine the Inverse Laplace transform of following functions $F(s)$; 6

i) $F(s) = \frac{3}{s(s^2 + 6s + 9)}$

ii) $F(s) = \frac{2(s+1)}{(s+2)(s+3)}$

OR

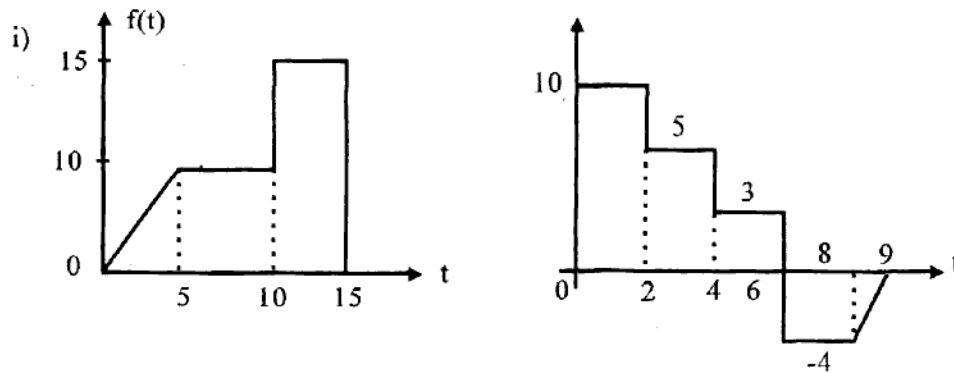8. a) Obtain the Laplace transform for following waveforms. 7




- b) Obtain initial value and final value of $f(t)$: 6

$$F(s) = \frac{17s^3 + 18s + 6s + 5}{s^5 + 4s^4 + 3s^3 + 5s^2 + 18s}$$


9. a) State and explain maximum power transfer theorem and derive the conditions. 7

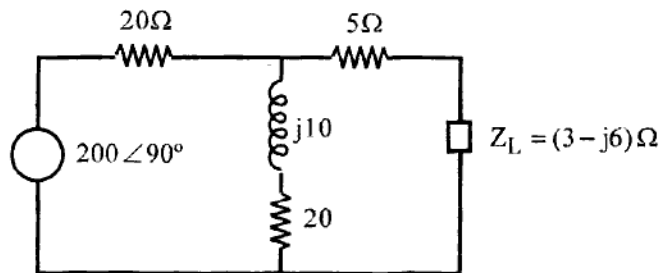- b) Find the current through Z_L by Thevenin's theorem shown in figure. 6




OR

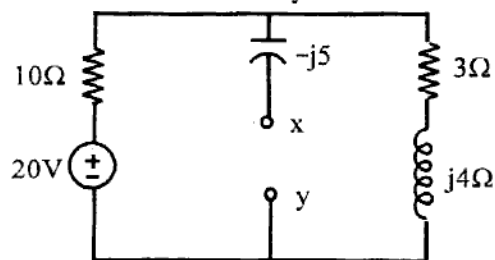10. a) Obtain the Norton's equivalent ckt at terminals xy shown below. 6



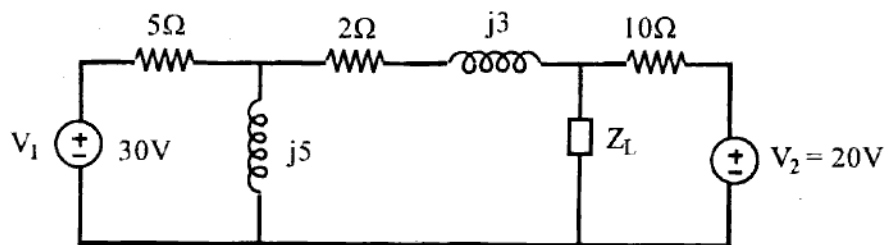
- b) By superposition theorem calculate current through " Z_L ". 7



$$(Z_L = 10 - 2j)$$

11. Determine the Z and Y parameters of n/w shown in figure.


14

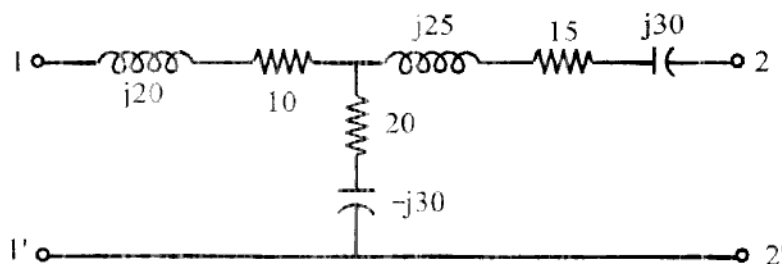

OR

12. a) Two identical section of network shown in fig. are connected in parallel, Obtain Y – parameter of resulting network.

7

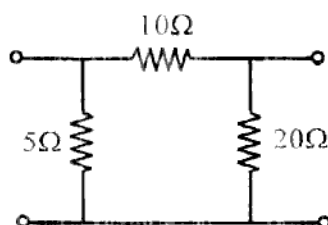

- b) Determine the h-parameters with following data.

7

- With o/p shorted (s/c) $V_1 = 25V$, $I_1 = 1A$, $I_2 = 2A$
- With i/p terminals open-circuited (o/c) $V_1 = 10V$, $V_2 = 50V$, $I_2 = 2A$
