

M.Sc. (Part-II) Semester-III (CBCS) Examination
ELECTRONICS
(Power Electronics)
Paper-3 ELE 2

Time : Three Hours]

[Maximum Marks : 80

Note :—(1) All questions are compulsory.

(2) Draw neat sketches wherever necessary.

EITHER

- | | | |
|----|--|---|
| 1. | (a) Explain interdisciplinary nature of Power Electronics. | 6 |
| | (b) Draw block diagram of Power Electronic System. | 4 |
| | (c) Explain efficiency and reliability in Power Electronics. | 6 |

OR

- | | | |
|--|--|---|
| | (p) Explain Total harmonic distortion and Power Factor in Power Electronics. | 8 |
| | (q) Explain thermal management in detail. | 4 |
| | (r) Write applications of Power Electronics. | 4 |

EITHER

- | | | |
|----|---|---|
| 2. | (a) Explain construction and working of SCHOTTKY DIODE. | 8 |
| | (b) Explain construction and working of MOSFET. | 8 |

OR

- | | | |
|--|---|---|
| | (p) Explain construction and working of SCR. | 8 |
| | (q) Explain ideal requirement of Power Electronics Devices. | 6 |
| | (r) Write applications of TRIAC. | 2 |

EITHER

- | | | |
|----|---|---|
| 3. | (a) Explain construction and working of single phase Bridge Rectifier with R.L. Load. | 8 |
| | (b) Explain construction and working of single phase Bidirectional controller with R.L. Load. | 8 |

OR

- | | | |
|--|---|---|
| | (p) Compare between PWM and Resonant convertors. | 4 |
| | (q) Explain construction and working of three phase Bidirectional controller. | 8 |
| | (r) What is cyclo convertor ? | 4 |

EITHER

4. (a) Explain construction and working of step up chopper with R.L. Load. 8
(b) Explain modulation technique of inverter. 8

OR

- (p) Explain construction and working of single phase inverter. 8
(q) Explain construction and working of step down chopper with R.L. Load. 8

EITHER

5. (a) Explain Buck, Boost and Buck-Boost Regulators. 8
(b) Explain types of motor drives and equivalent circuit. 8

OR

- (p) What is SMPS ? Explain any one type of SMPS. 8
(q) Explain Torque-speed characteristics of motor. 8