

- (R) Using D-type flipflop, organize 4-bit left shift SISO register and explain its working. 8

5. (A) What is the difference between volatile and nonvolatile memory ? 4
- (B) What is ROM ? Enlist its applications. 6
- (C) Using 7489 IC (16x4 RAM) arrange memory organization of 32x4 6

OR

- (P) What is EPROM ? Explain its applications. 4
- (Q) What do you mean by memory map for data processor system ? 4
- (R) Explain the function of 6264 IC to obtain 8KB memory. 8



Third Semester M.Sc. (Part - II) Physics
(CBCS Pattern) Examination

DIGITAL TECHNIQUES

Paper : 3 PHY 4-(i)

P. Pages : 4

Time : Three Hours]

[Max. Marks : 80

- Note :** (1) All questions are compulsory and carry equal marks.
(2) Draw neat diagrams wherever necessary.

1. (A) Define-Fan in, Fan out, Propagation Delay and noise margin of a digital functional device. 4
- (B) How C-MOS device is different from standard TTL device ? 4
- (C) Draw a circuit of N-MOS NAND Gate and explain construction and working with truth table. 8

OR

- (P) Show that NAND gate can be used as universal logic gate. 4
- (Q) What is NOT function ? Draw circuit diagram for C-MOS NOT Gate and explain its working with truth table. 8

- (R) How a low power and high power Schottky TTL devices are distinguished ? 4

2. (A) Write down Boolean laws for simplification of logic circuit and explain how these laws are effective in reducing Boolean algebraic expressions with suitable example. 12

- (B) Reduce the following expression using Boolean algebraic method.

$$Y = ABC + \bar{A}BC + A\bar{B}C + AB\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C}$$

4

OR

- (P) Draw the block diagram of Internal circuit of 7483 IC. By using 7486 IC how a 2's complement of a given number is obtained ? 8

- (Q) Draw neat circuit diagram for 4-bit binary multiplier using 7483 and 7408 IC's. 8

3. (A) Draw circuit diagram of 4:1 multiplexer using basic gates. 4

- (B) Using two blocks of 4:1 multiplexer how one can obtain 8:1 operation. 4

- (C) What are encoders and decoders ? Explain the working of 74138 IC with the internal circuit diagram. 8

OR

- (P) Give salient features of 74181 (4-bit ALU). 4

- (Q) Explain the operation of LED and how it can be used to display alpha-numeric characters. 6

- (R) How HEX-code is obtained for display of characters ? 6

4. (A) What is flip-flop ? State its important applications. 4

- (B) Explain the working of JKMS flip-flop and draw neat diagram using NAND gates. 8

- (C) Using 7493 IC, show how it can be used as Mod-7 counter. 4

OR

- (P) What are synchronous and asynchronous counters ? 4

- (Q) Explain the working of Ring counter. 4